
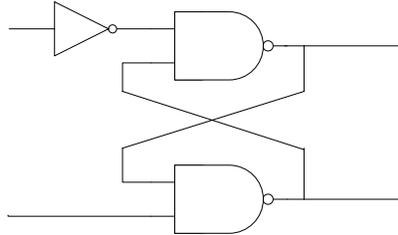


# EECS 270

## Homework #7


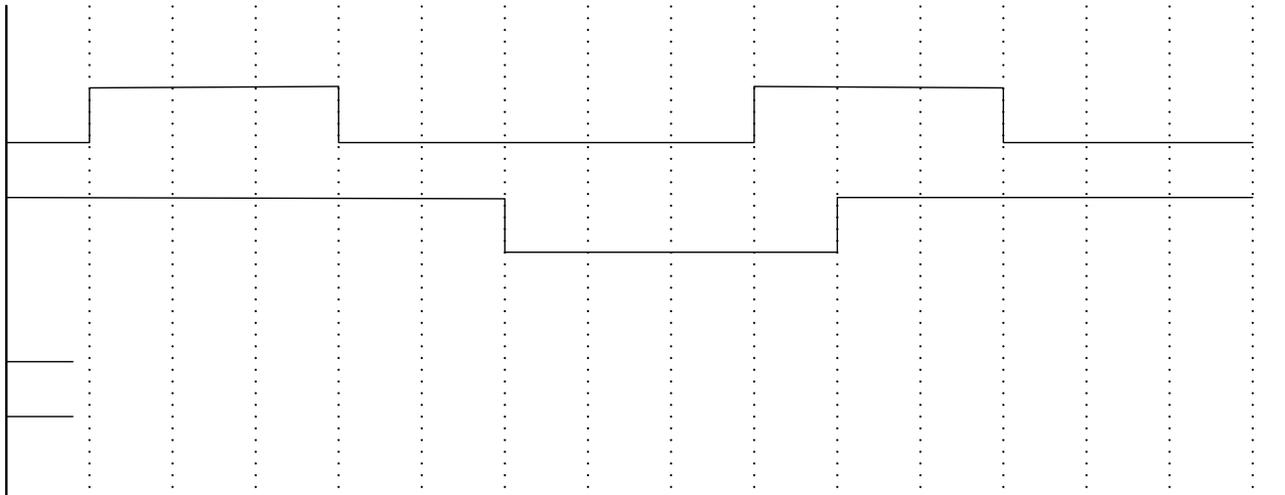


1. (a) Using the above circuit, and given the waveforms for inputs X and Y below, complete the waveforms for Q and QB. Assume the delay of each gate is 1ns. Show all causality arrows. (4)



- (b) For what values of inputs X and Y are the outputs Q and QB not complements of each other? (2)

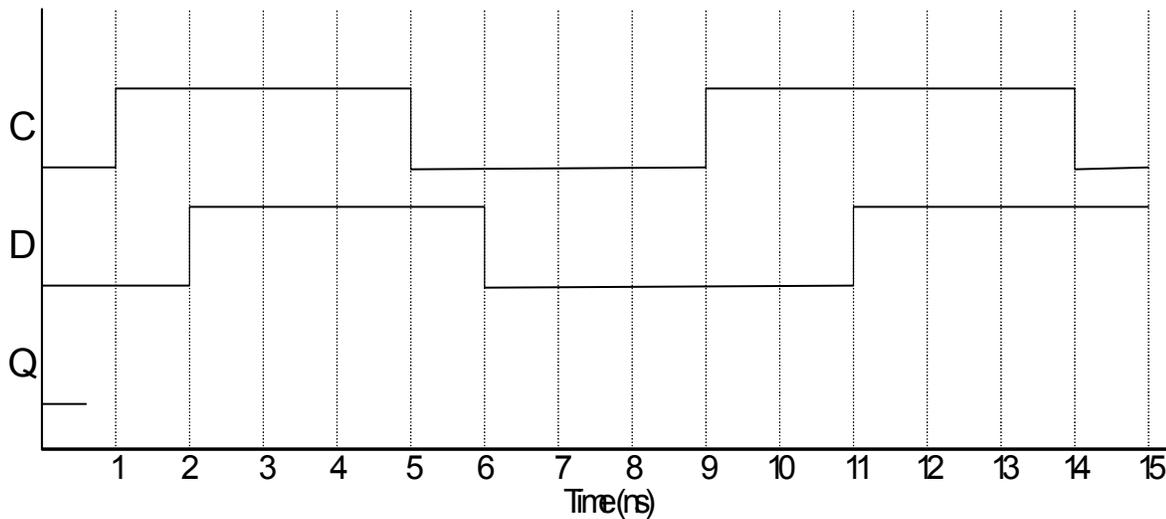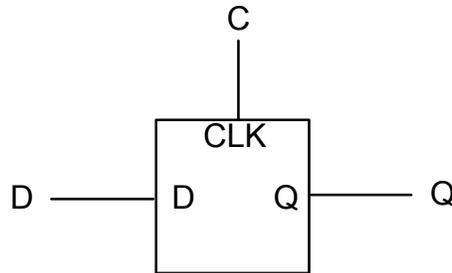2. (a) Complete the following timing diagram for the D latch below. Assume that for this latch,  $t_{\text{CLK} \rightarrow \text{Q}}^{\text{pHL}} = t_{\text{CLK} \rightarrow \text{Q}}^{\text{pLH}} = 1\text{ns}$  (latch delay from input CLK to Q), and  $t_{\text{D} \rightarrow \text{Q}}^{\text{pHL}} = t_{\text{D} \rightarrow \text{Q}}^{\text{pLH}} = 2\text{ns}$  (latch delay from input D to Q). **(3)**



3. Consider a chain of six scan flip-flops: SF1 through SF6, connected as follows:

$TI \rightarrow SF1 \rightarrow SF2 \rightarrow SF3 \rightarrow SF4 \rightarrow SF5 \rightarrow SF6 \rightarrow TO$

(a) How many cycles with  $TE = 1$  are needed to read the states of all flip-flops? **(1)**

(b) If SF2 is broken (i.e., has a manufacturing fault), how many cycles with  $TE = 1$  are necessary to detect this with one test vector? (Do not include the cycles needed to scan in the test pattern). **(1)**

(c) Is it possible to reliably say whether SF2 is broken by comparing the output bits read off TO with what's expected when there are no faults? **(1)**

4. Given the J-K flip-flop below, hook up the inputs (adding any necessary gates) such that it behaves logically like a negative-edge triggered D flip-flop, also shown below. (3)

