

EECS 312: Digital Integrated Circuits

Homework #1 Solutions

1. IC Cost and Economics:

- a) The general process for part A, is to calculate the dies/wafer, then the yield, cost of die, variable cost, followed by the cost per IC for both designs on both fabrication facilities. The **ASIC design should be fabricated in the 4 inch facility** and the **Microprocessor (uproc) should be fabricated in the 8 inch facility**.

$$\frac{\text{Dies}}{\text{Wafer}}_{(\text{general eq.})} = \frac{\pi \left(\frac{\text{Wafer Size}}{2} \right)^2}{\text{Die Area}} - \frac{\pi(\text{Wafer Size})}{\sqrt{2}(\text{Die Area})}$$

$$\frac{\text{Dies}}{\text{Wafer}}_{(4\text{inch,uproc})} = \frac{\pi \left(\frac{(10.16\text{cm})}{2} \right)^2}{3.2\text{cm}^2} - \frac{\pi(10.16\text{cm})}{\sqrt{2}(3.2\text{cm}^2)}$$

$$\frac{\text{Dies}}{\text{Wafer}}_{(4\text{inch,uproc})} = 12$$

$$\frac{\text{Dies}}{\text{Wafer}}_{(4\text{inch,ASIC})} = 279$$

$$\frac{\text{Dies}}{\text{Wafer}}_{(8\text{inch,uproc})} = 76$$

$$\frac{\text{Dies}}{\text{Wafer}}_{(8\text{inch,ASIC})} = 1206$$

$$\text{Cost of Die}_{(\text{general eq.})} = \frac{\text{Cost of Wafer}}{\text{Yield} \times \frac{\text{Dies}}{\text{Wafer}}}$$

$$\text{Cost of Die}_{(4\text{inch,uproc})} = \frac{\$150.00}{0.2773 \times 12}$$

$$\text{Cost of Die}_{(4\text{inch,uproc})} = \$45.06$$

$$\text{Cost of Die}_{(4\text{inch,ASIC})} = \$0.61$$

$$\text{Cost of Die}_{(8\text{inch,uproc})} = \frac{\$800.00}{0.2453 \times 76}$$

$$\text{Cost of Die}_{(8\text{inch,uproc})} = \$42.90$$

$$\text{Cost of Die}_{(8\text{inch,ASIC})} = \$0.76$$

$$\text{Yield}_{(\text{general eq.})} = \left(1 + \frac{\text{Die Area} \times \text{Defect Density}}{\alpha} \right)^{-\alpha}$$

$$\text{Yield}_{(4\text{inch,uproc})} = \left(1 + \frac{(3.2\text{cm}^2) \times 0.5\text{cm}^{-2}}{3} \right)^{-3}$$

$$\text{Yield}_{(4\text{inch,uproc})} = 0.2773$$

$$\text{Yield}_{(4\text{inch,ASIC})} = 0.8847$$

$$\text{Yield}_{(8\text{inch,uproc})} = 0.2453$$

$$\text{Yield}_{(8\text{inch,ASIC})} = 0.8721$$

$$\text{Variable Cost}_{(\text{general})} = \frac{\text{Die} + \text{Packaging} + \text{Testing}}{\text{Functional Test Yield}}$$

$$\text{Variable Cost}_{(4\text{inch,uproc})} = \frac{45.06 + 25.00 + 2.78}{0.95}$$

$$\text{Variable Cost}_{(4\text{inch,uproc})} = \$76.68$$

$$\text{Variable Cost}_{(4\text{inch,ASIC})} = \$2.07$$

$$\text{Variable Cost}_{(8\text{inch,uproc})} = \frac{42.90 + 25.00 + 2.78}{0.95}$$

$$\text{Variable Cost}_{(8\text{inch,uproc})} = \$74.40$$

$$\text{Variable Cost}_{(8\text{inch,ASIC})} = \$2.23$$

$$\text{Cost per IC}_{(general)} = \text{Variable Cost of IC} + \left(\frac{\text{Fixed NRE Cost}}{\text{Volume}} \right)$$

$$\text{Cost per IC}_{(4inch,uproc)} = \$76.68 + \left(\frac{\$200,000,000}{50,000,000} \right) = \$80.68$$

$$\text{Cost per IC}_{(4inch,ASIC)} = \$2.07 + \left(\frac{\$2,000,000}{1,000,000} \right) = \$4.07$$

$$\text{Cost per IC}_{(8inch,uproc)} = \$74.40 + \left(\frac{\$200,000,000}{50,000,000} \right) = \$78.40$$

$$\text{Cost per IC}_{(4inch,uproc)} = \$2.23 + \left(\frac{\$2,000,000}{1,000,000} \right) = \$4.23$$

b) In part b, a new 12 inch facility is proposed, and the microprocessor design is being considered for the new facility. We must solve for a constraint on the defect density of the new fab such that the 12 inch fab would result in cost savings over the previous fabrication selection in part A (8 inch fab). The first thing we know is that the best cost per IC from the 8 inch fab is \$78.40.

$$\text{Cost per IC}_{(uproc)} \geq \text{Variable Cost} + \left(\frac{\text{Fixed Cost}}{\text{Volume}} \right)$$

$$\$78.40 \geq \text{Variable Cost} + \left(\frac{(\$1,000,000,000 + \$200,000,000)}{50,000,000} \right)$$

$$\text{Variable Cost} \leq \$54.40$$

$$\$54.40 \geq \frac{\text{Die Cost} + \$25.00 + \$2.78}{0.95}$$

$$\text{Cost per Die} \leq \$23.90$$

$$\$23.90 \geq \frac{\text{Wafer Cost}}{\text{Yield} \times \frac{\text{Dies}}{\text{Wafer}}} = \frac{\$1500}{\text{Yield} \times 190}$$

$$\text{Yield} \geq 0.3303$$

$$0.3303 \leq \left(1 + \frac{(3.2 \text{ cm}^2) \times (\text{Defect Density})}{3} \right)^{-3}$$

$$\text{Defect Density} \leq 0.4187 \text{ cm}^{-2}$$

2. Capacitance Calculations:

a) First, calculate the area and perimeter of the drain regions.

$$\begin{aligned} AD(\text{area of drain})_{NMOS} &= (L_{drawn} * 2.5) * (W_n) \\ &= (0.25\mu\text{m})(2.5) * (4\mu\text{m}) = 2.5 \mu\text{m}^2 \end{aligned}$$

$$\begin{aligned} PD(\text{perimeter})_{NMOS} &= (2 * 2.5L_{drawn}) + W_n \\ &= (2 * 0.625\mu\text{m}) + 4\mu\text{m} = 5.25\mu\text{m} \end{aligned}$$

$$AD(\text{area of drain})_{PMOS} = (0.25\mu\text{m})(2.5) * (6\mu\text{m}) = 3.75 \mu\text{m}^2$$

$$PD(\text{perimeter})_{PMOS} = (2 * 0.625\mu\text{m}) + 6\mu\text{m} = 7.25\mu\text{m}$$

For C_{db} calculations, consider a $0 \rightarrow V_{DD}$ and $V_{DD} \rightarrow 0$ transition on the drain. Since we care about 50% delay, this translates to $0 \rightarrow V_{DD}/2$ and $V_{DD} \rightarrow V_{DD}/2$ transitions on the drain.

For $0 \rightarrow V_{DD}/2$ Transition:

NMOS

Bulk is held to ground, so at $V_{drain} = 0$, we have the zero-bias case. As V_{drain} increases the depletion region grows and C_j decreases.

Calculate K_{eq} for this transition:

$V_{high} = -1V$ and $V_{low} = 0V$ (negative due to reverse bias).


$$K_{eq}(NMOS, lh) = \frac{-(0.9)^{0.5}}{((-1)-0)(1-0.5)} \left[((0.9)-(-1))^{0.5} - ((0.9)-0)^{0.5} \right] = 0.815$$

$$K_{eqsw}(NMOS, lh) = \frac{-(0.9)^{0.44}}{((-1)-0)(1-0.44)} \left[((0.9)-(-1))^{0.56} - ((0.9)-0)^{0.56} \right] = 0.835$$

PMOS

Bulk is held to V_{DD} , so when $V_{drain}=0$, we actually have a large reverse bias across the bulk-drain junction.

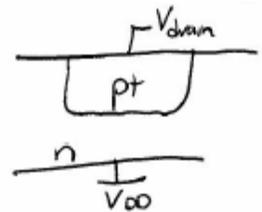$V_{high} = -2V$ and $V_{low} = -1V$ since the bias across the junction changes from $-2V$ to $-1V$ as the drain transitions from 0 to $V_{DD}/2$.



$$K_{eq}(PMOS, lh) = \frac{-(0.9)^{0.48}}{((-2)-(-1))(1-0.48)} \left[((0.9)-(-2))^{0.52} - ((0.9)-(-1))^{0.52} \right] = 0.627$$

$$K_{eqsw}(PMOS, lh) = \frac{-(0.9)^{0.32}}{((-2)-(-1))(1-0.32)} \left[((0.9)-(-2))^{0.68} - ((0.9)-(-1))^{0.68} \right] = 0.733$$

$$\begin{aligned} C_{db}(NMOS, lh) &= AD_{NMOS} * C_j * K_{eq} + PD_{NMOS} * C_{jsw} * K_{eqsw} \\ &= (2.5 \text{ } \mu\text{m}^2) (2 \times 10^{-3} \text{ F/m}^2) (0.815) + (5.25 \text{ } \mu\text{m}) (2.8 \times 10^{-10} \text{ F/m}) (0.835) \\ &= 5.30245 \text{ fF} \end{aligned}$$

$$\begin{aligned} C_{db}(PMOS, lh) &= AD_{PMOS} * C_j * K_{eq} + PD_{PMOS} * C_{jsw} * K_{eqsw} \\ &= (3.75 \text{ } \mu\text{m}^2) (1.9 \times 10^{-3} \text{ F/m}^2) (0.627) + (7.25 \text{ } \mu\text{m}) (2.2 \times 10^{-10} \text{ F/m}) (0.733) \\ &= 5.63651 \text{ fF} \end{aligned}$$

For $V_{DD} \rightarrow V_{DD}/2$ Transition:

NMOS

Calculate K_{eq} for this transition:

$V_{high} = -2V$ and $V_{low} = -1V$ (negative due to reverse bias).

$$K_{eq}(NMOS, hl) = \frac{-(0.9)^{0.5}}{((-2)-(-1))(1-0.5)} \left[((0.9)-(-2))^{0.5} - ((0.9)-(-1))^{0.5} \right] = 0.616$$

$$K_{eqsw}(NMOS, hl) = \frac{-(0.9)^{0.44}}{((-2)-(-1))(1-0.44)} \left[((0.9)-(-2))^{0.56} - ((0.9)-(-1))^{0.56} \right] = 0.653$$

Note that these values are 25-30% smaller than those for the $0 \rightarrow VDD$ transition. This is because in the $VDD \rightarrow 0$ transition the NMOS drain-bulk junction has a larger reverse bias on it leading to a smaller average capacitance (this is only true since we restrict our attention to the first half of the transition).

PMOS

$$V_{high} = -1V \text{ and } V_{low} = 0V$$

$$K_{eq}(PMOS, hl) = \frac{-(0.9)^{0.48}}{((-1)-(0))(1-0.48)} \left[((0.9)-(-1))^{0.52} - ((0.9)-(0))^{0.52} \right] = 0.822$$

$$K_{eqsw}(PMOS, hl) = \frac{-(0.9)^{0.32}}{((-1)-(0))(1-0.32)} \left[((0.9)-(-1))^{0.68} - ((0.9)-(0))^{0.68} \right] = 0.876$$

The K_{eq} values are larger than in the $0 \rightarrow VDD/2$ transition, since the reverse bias over the junction is less in this case.

$$\begin{aligned} C_{db}(NMOS, hl) &= AD_{NMOS} * C_j * K_{eq} + PD_{NMOS} * C_{jsw} * K_{eqsw} \\ &= (2.5 \text{ } \mu\text{m}^2) (2 \times 10^{-3} \text{ F/m}^2) (0.616) + (5.25 \text{ } \mu\text{m}) (2.8 \times 10^{-10} \text{ F/m}) (0.653) \\ &= 4.03991 \text{ fF} \end{aligned}$$

$$\begin{aligned} C_{db}(PMOS, hl) &= AD_{PMOS} * C_j * K_{eq} + PD_{PMOS} * C_{jsw} * K_{eqsw} \\ &= (3.75 \text{ } \mu\text{m}^2) (1.9 \times 10^{-3} \text{ F/m}^2) (0.822) + (7.25 \text{ } \mu\text{m}) (2.2 \times 10^{-10} \text{ F/m}) (0.876) \\ &= 7.25397 \text{ fF} \end{aligned}$$

Gate-Channel Capacitance (C_{GC}):

$$\begin{aligned} C_{gc}(NMOS) &= C_{ox} W L_{eff} \\ &= \left(\frac{\epsilon_{ox}}{t_{ox}} \right) W_n (0.8 * L_{drawn}) = \left(\frac{3.9 \epsilon_o}{(5.75E-7 \text{ cm})} \right) (4E-4 \text{ cm}) (0.2E-4 \text{ cm}) \\ &= 4.804 \text{ fF} \end{aligned}$$

$$\begin{aligned} C_{gc}(PMOS) &= \left(\frac{\epsilon_{ox}}{t_{ox}} \right) W_p (0.8 * L_{drawn}) = \left(\frac{3.9 \epsilon_o}{(5.75E-7 \text{ cm})} \right) (6E-4 \text{ cm}) (0.2E-4 \text{ cm}) \\ &= 7.206 \text{ fF} \end{aligned}$$

Gate-Drain Overlap Capacitance (C_{GD}):

The intended way to calculate this was to use the SPICE Model parameter C_{GD0} to calculate the overlap capacitance in a simple manner. If you used C_{ox} method of calculating the overlap capacitance you may have obtained different figures (you will still receive credit). The SPICE model was modified from a previous technology generation to reflect our default technology and is not valid for every calculation.

$$\begin{aligned}
C_{gd}(NMOS) &= C_{gd0}W_n \\
&= (3.1 \times 10^{-10} \text{ F/m})(4\mu\text{m}) = 1.24 \text{ fF} \\
C_{gd}(PMOS) &= C_{gd0}W_p \\
&= (2.7 \times 10^{-10} \text{ F/m})(6\mu\text{m}) = 1.62 \text{ fF}
\end{aligned}$$

b) Layout Issues: The idea behind the two layout diagrams is to illustrate the manner of calculating the area and perimeter of the transistor in our equations for capacitance. In the conventional layout, we use the equations from the solution above. For the folded layout, one can see that the drain region (the center strip in the diagram) has a significantly reduced area. So we can begin by recalculating the areas and perimeters for the C_{db} calculation.

$$\begin{aligned}
AD(\text{area of drain})_{NMOS} &= (L_{drawn} * 2.5) * \left(\frac{W_n}{2}\right) \\
&= (0.25\mu\text{m})(2.5) * (2\mu\text{m}) = 1.25 \mu\text{m}^2 \\
PD(\text{perimeter})_{NMOS} &= (2 * 2.5L_{drawn}) \\
&= (2 * 0.625\mu\text{m}) = 1.25 \mu\text{m}
\end{aligned}$$

According to our methods, the area is reduced in half, as the width of each device in this “parallel configuration” is half of the previous width. The perimeter is greatly reduced, since both “Width” edges are conducting regions (not counted).

$$\begin{aligned}
C_{db}(NMOS, hl) &= AD_{NMOS} * C_j * K_{eq} + PD_{NMOS} * C_{jsw} * K_{eqsw} \\
&= (1.25 \mu\text{m}^2)(2 \times 10^{-3} \text{ F/m}^2)(0.616) + (1.25 \mu\text{m})(2.8 \times 10^{-10} \text{ F/m})(0.653) \\
&= 1.76855 \text{ fF} \\
C_{gc}(NMOS) &= C_{ox}W_2L_{eff} + C_{ox}W_2L_{eff} \\
&= \left(\frac{\epsilon_{ox}}{t_{ox}}\right) 2W_2(0.8 * L_{drawn}) = \left(\frac{3.9\epsilon_o}{(5.75E-7 \text{ cm})}\right) 2(2E-4 \text{ cm})(0.2E-4 \text{ cm}) \\
&= 4.804 \text{ fF} \\
C_{gd}(NMOS) &= C_{gd0}W_2 + C_{gd0}W_2 \\
&= (3.1 \times 10^{-10} \text{ F/m})2(2\mu\text{m}) = 1.24 \text{ fF}
\end{aligned}$$

The folded layout results in a 56% reduction in the C_{db} capacitance, but the other capacitances remain the same (since there is still 4um worth of gate width). In reality, the width of the drain is slightly greater in the folded layout (greater than $2.5 L_{drawn}$), but the folded layout usually results in a significant savings in C_{db} capacitance.

The folded layout will lead to a slightly faster circuit (delay and rise times) and slightly less power consumption. The folded layout also appears to be more compact and manageable (as it is in many process technologies), but this is ultimately up to the design rules of a particular technology – not a blanket statement.

3. RC Network Review:

a) First one must determine the time for a clock cycle, realize that the final voltage is 0 and 95% of the final voltage is $(2.5-0)*0.05 = 0.125V$.

$$t_{period} = \frac{1}{1.2GHz} = 833.33 ps$$

$$V_{final} = V_{initial} e^{-t/RC}$$

$$0.05 = e^{-t_{period} / R(3*24.4 fF)}$$

$$\ln(0.05) = \frac{-t_{period}}{R_{eq}(73.2 fF)}$$

$$-2.9957 = \frac{-833.33 ps}{R_{eq}(73.2 fF)}$$

$$R_{eq} = 3800 \Omega$$

- b) If the capacitance is increased to $3(28.3 fF) = 84.9 fF$, we must calculate the time required to reach the 0.125V voltage point. The calculation below shows that the circuit will still operate within a clock cycle at 1GHz.

$$t_{period} = \frac{1}{1.2GHz} = 833.33 ps$$

$$V_{final} = V_{initial} e^{-t/RC}$$

$$0.125V = 2.5e^{-t/RC}$$

$$\ln(0.05) = \frac{-t_{period}}{(3800\Omega)(84.9 fF)}$$

$$t_{period} = 966.48 ps$$

$$t_{period} < \frac{1}{1GHz} = 1000 ps$$

4. Unified I-V Model:

- a) This is a PMOS device.

- b) Using measurements 1 & 4, $V_{T0} = -0.5 V$.

$$\frac{I_{D1}}{I_{D4}} = \frac{k \frac{W}{L} \left(V_{GT1} V_{min1} - \frac{V_{min1}^2}{2} \right) (1 + \lambda V_{DS1})}{k \frac{W}{L} \left(V_{GT4} V_{min4} - \frac{V_{min4}^2}{2} \right) (1 + \lambda V_{DS4})}$$

$$1.5 = \frac{\left((-2.5 - V_{T0})(-1) - \frac{(-1)^2}{2} \right) (1 + \lambda 2.5)}{\left((-2.0 - V_{T0})(-1) - \frac{(-1)^2}{2} \right) (1 + \lambda 2.5)}$$

$$2.25 + 1.5V_{T0} = 2 + V_{T0}$$

$$V_{T0} = -0.5V$$

c) Using measurements 1 & 5, $\gamma = -0.44897 \text{ V}^{1/2}$

$$\frac{I_{D1}}{I_{D5}} = \frac{k \frac{W}{L} \left(V_{GT1} V_{\min 1} - \frac{V_{\min 1}^2}{2} \right) (1 + \lambda V_{DS1})}{k \frac{W}{L} \left(V_{GT5} V_{\min 5} - \frac{V_{\min 5}^2}{2} \right) (1 + \lambda V_{DS5})}$$

$$1.171875 = \frac{\left((-2.5 - (-0.5))(-1) - \frac{(-1)^2}{2} \right) (1 + \lambda 2.5)}{\left((-2.5 - (-0.5 + \gamma(4903)))(-1) - \frac{(-1)^2}{2} \right) (1 + \lambda 2.5)}$$

$$1.171875((2.0 - 0.49\gamma) - 0.5) = 1.5$$

$$\gamma = -0.44897 \text{ V}^{1/2}$$

d) Using measurements 1 & 6, $\lambda = -0.05 \text{ V}^{-1}$

$$\frac{I_{D1}}{I_{D6}} = \frac{k \frac{W}{L} \left(V_{GT1} V_{\min 1} - \frac{V_{\min 1}^2}{2} \right) (1 + \lambda V_{DS1})}{k \frac{W}{L} \left(V_{GT6} V_{\min 6} - \frac{V_{\min 6}^2}{2} \right) (1 + \lambda V_{DS6})}$$

$$1.0465 = \frac{\left((-2.5 - V_{T0})(-1) - \frac{(-1)^2}{2} \right) (1 + \lambda(-2.5))}{\left((-2.5 - V_{T0})(-1) - \frac{(-1)^2}{2} \right) (1 + \lambda(-1.5))}$$

$$1.0465(1 + \lambda(-1.5)) = (1 + \lambda(-2.5))$$

$$\lambda = -0.05 \text{ V}^{-1}$$

- e) 1 → Saturation
 2 → Cutoff
 3 → Saturation
 4 → Saturation
 5 → Saturation
 6 → Saturation
 7 → Linear