

EECS 312: Digital Integrated Circuits

Homework #8 Solutions

1. Interconnect and Scaling:

a. What is the total **capacitance** of this wire? Use three models:

- The simple rule of thumb yields **2 pF/cm * 1.4cm = 2.8 pF**
- Using the detailed equation:

$$C_{wire} = 3.9(8.854E-14) \left[\left(\frac{1.5}{0.5} \right) + 0.77 + 1.06 \left(\frac{1.5}{0.5} \right)^{0.25} + 1.06 \left(\frac{0.8}{0.5} \right)^{0.5} \right] = 2.247 \text{ pF/cm}$$

$$C_{wire} = 2.247 \text{ pF/cm} (1.4 \text{ cm}) = 3.145 \text{ pF}$$

iii. Use table 4-2 from Rabaey...

$$\begin{aligned} C_{total} &= C_{pp} + C_{fringe} \\ &= (1.5 \text{ um})(14,000 \text{ um})(38 \text{ aF/um}^2) + 2(52 \text{ aF/um})(14,000 \text{ um}) \\ &= 798 \text{ fF} + 1456 \text{ fF} \\ &= 2.254 \text{ pF} \end{aligned}$$

b. What is the total **resistance** of the wire?

i. Aluminum (Al)

$$R_{sheet} = \frac{\rho}{H_{wire}} = \frac{2.7E-8}{0.8 \text{ um}} = 0.03375 \Omega$$

$$R_{total} = R_{sheet} \frac{L}{W} = R_{sheet} \frac{14,000}{1.5} = 315 \Omega$$

ii. Copper (Cu)

$$R_{sheet} = \frac{\rho}{H_{wire}} = \frac{1.7E-8}{0.8 \text{ um}} = 0.02125 \Omega$$

$$R_{total} = R_{sheet} \frac{L}{W} = R_{sheet} \frac{14,000}{1.5} = 198.33 \Omega$$

c. Using the detailed delay model from class, we consider any term with r_w to be due to wire resistance.

$$C_{int} = 0.6 \text{ fF/um} (30 \text{ um}) = 18 \text{ fF}$$

$$C_{wire} = 3.145 \text{ pF}$$

$$C_{load} = 6(6 \text{ fF/um}^2)(0.2 \text{ um})(30 \text{ um}) = 216 \text{ fF}$$

$$r_w = 0.0225 \Omega/\text{um}$$

$$c_w = 0.2246 \text{ fF/um}$$

$$R_d = 0.8 \left(\frac{2.5}{10(731E-6)} \right) = 273.6 \Omega$$

$$t_{phi} = 0.69 R_d (18 + 3145 + 216 \text{ fF}) + 0.38(315)(3145 \text{ fF}) + 0.69(315)(216 \text{ fF})$$

$$= 637.9 \text{ ps} + 376.5 \text{ ps} + 46.9 \text{ ps} = 1.06 \text{ ns}$$

40% due to r_{wire}

d. Scale two generations. $S^2 = \sim 2$, assuming 2.

$$\begin{aligned} t_{phl}(scaled) &= 0.69(R_d) \left(\frac{C_{int}}{S^2} + C_{wire} + \frac{C_{gate}}{S^2} \right) + 0.38(S^4 R_{wire})(C_{wire}) + 0.69(S^4 R_{wire}) \left(\frac{C_{gate}}{S^2} \right) \\ &= 0.69(273.6)(9 fF + 3145 fF + 108 fF) + 0.38(793)(3145 fF) + 0.69(793)(108 fF) \\ &= 615.8 ps + 948.1 ps + 59.1 ps = 1.62 ns \\ &62\% \text{ due to } r_{wire} \text{ (despite Copper)} \end{aligned}$$

2. Repeater Design:

a. Use the tapered buffering approach to driving this wire for optimal delay...

$$C_{in} = (3um)(6 fF / um^2)(0.2um) = 3.6 fF$$

$$C_L = C_{wire} + C_{load} = 3.145 pF + 216 fF$$

$$F = \frac{3.361 pF}{3.6 fF} = 933.6$$

$$f_{opt} \approx 3.6 \rightarrow N = \frac{\log(933.6)}{\log(3.6)} = 5.339$$

$$t_{p0} = 0.69(0.5) \left(0.8 \left(\frac{2.5}{731} \right) + 0.8 \left(\frac{2.5}{2(300)} \right) \right) (3.6 fF) = 7.538 ps$$

$$t_{p0}(5) = (5)(7.538 ps) \left(1 + \sqrt[5]{933.6} \right) + 0.38(315)(3.145 pF) + 0.69(315)(216 fF) = 609.1 ps$$

$$t_{p0}(6) = (6)(7.538 ps) \left(1 + \sqrt[6]{933.6} \right) + 0.38(315)(3.145 pF) + 0.69(315)(216 fF) = 610.1 ps$$

$$W_{total}(5) = \left(\frac{f^N - 1}{f - 1} \right) A_{unit} = \left(\frac{3.93^5 - 1}{2.93} \right) (3um)(0.25um) = 239.7 um^2$$

b. Use the repeater insertion technique (pg. 466-467) to optimize delay. Use the detailed approach of 9.9 and 9.10 in the text. Find the optimal delay and the total area of the transistors used in the repeater based design.

$$R_d = 0.8(0.5) \left(\frac{2.5}{731} + \frac{2.5}{2(300)} \right) = 3034 \Omega$$

$$C_d = 3.6 fF$$

$$m_{opt} = L \sqrt{\frac{0.38rc}{0.69R_d C_d (\gamma + 1)}} = 14,000 \sqrt{\frac{0.38(0.0225)(0.2246 fF)}{0.69(3034)(3.6 fF)(2)}}$$

$$m_{opt} = 4.99$$

$$s_{opt} = \sqrt{\frac{R_d c}{r C_d}} = 91.72$$

$$t_p = 4 \left(0.69 \frac{3034}{91.72} \left(91.7(3.6 fF) + \frac{3.145 pF}{5} + 91.7(3.6 fF) \right) + 0.69 \left(\frac{315}{5} \right) (91.7(3.6 fF)) + 0.38(0.225)(0.0225)(2800)^2 \right)$$

$$+ \left(0.69 \frac{3034}{91.7} \left(91.7(3.6 fF) + \frac{3.145 pF}{5} + 216 fF \right) + 0.69 \left(\frac{315}{5} \right) (216 fF) + 0.38(0.225)(0.0225)(2800)^2 \right)$$

$$t_p = 286.64 ps$$

$$W_{total} = 5(91.72)(3um)(0.25um) = 343.95 um^2$$

- c. This comparison is not completely even, since in (a), the input capacitance is held fixed to a $3\mu\text{m}$ gate. In (b), the input capacitance of the repeater chain is allowed to be very large, $91.72\times$ the input cap of (a). Therefore the delay comparison is not appropriate, since the repeater chain loads the previous stage more than the tapered buffer chain. An appropriate comparison could be made by creating a small tapered buffer chain for the input of the repeater setup.