

# EECS 312: Digital Integrated Circuits

## Homework #1

Reading: Section 1.3, 3.2.3, 3.3 of Rabaey

1. a) An electronic design company is preparing to launch two new products, a high-performance, high-volume microprocessor and a low-volume ASIC unit. Several fabrication facilities implementing the desired technology are available to them, including a 4-inch wafer fab and an 8-inch wafer fab. Calculate the *cost per IC* of each design at each fabrication plant (4 calculations, 2 per 4-inch and 2 per 8-inch). Identify the minimum cost fabrication facility for each design.

The microprocessor die size is  $3.2 \text{ cm}^2$  and the projected volume is 50,000,000 units over the lifetime of the product. The cost of packaging the microprocessor is \$25.00 per part, cost of testing per part is \$2.78, and the non-recurring engineering design cost is \$200,000,000.00. The ASIC design is  $0.25 \text{ cm}^2$  and the projected volume is only 1,000,000 units. The cost of packaging the ASIC is \$0.67, cost of testing is \$0.69, and the design cost is \$2,000,000.00. For both designs, the functional test yield rate is 95% and  $\alpha=3$ . Information on the fabrication options is listed in the table below. (*Hint: Carry significant digits to ensure proper answers*)

Fabrication Facilities for Problem 1		
	4 Inch Fab	8 Inch Fab
Cost per Wafer	\$150.00	\$800.00
Wafer Size (in.)	4	8
Wafer Size (cm)	10.16	20.32
Defect Density ( $\text{cm}^{-2}$ )	0.5	0.56

- b) The operations department suggests studying the impact of transitioning to a new 12-inch fabrication facility for production of the microprocessor part. The 12-inch fabrication facility will cost an additional \$1,000,000,000.00 to construct for this project. Develop a constraint on the defect density of this new facility that will ensure cost savings over the previous minimum cost solution. Volume cost for 12-inch wafers is estimated to be \$1500/wafer.
2. a) Given the below SPICE model parameters, determine the junction capacitances  $C_{db}$ , the gate-to-channel capacitance, and the gate-to-drain overlap capacitances of both an NMOS and PMOS device, shown in Figure 2.1. Let  $W_n = 4\mu\text{m}$  and  $W_p = 6\mu\text{m}$  while  $L_{drawn} = 0.25\mu\text{m}$  and  $L_{eff} = 0.2\mu\text{m}$  for both N and P-type devices. Use an approximation that the length of the source/drain regions ( $L_s$  in Sec. 3.3 of text) is equal to  $2.5 \cdot L_{drawn}$ . To determine the voltage swing(s) of interest to calculate the junction capacitances, consider that the drain of both the NMOS and PMOS devices will swing from 0V to  $V_{dd}$  and from  $V_{dd}$  to 0.  $V_{dd}$  in this case is 2V and we are concerned with the capacitances relevant to 50% delay calculations. Therefore, you should have a total of 4  $C_{db}$  calculations, 2 each for NMOS and PMOS (See Table 2.1). Ignore the bias dependent nature of  $C_{gc}$  as mentioned in lecture. Units for and definitions of relevant SPICE parameters are provided in the Lecture Notes from 1/14 which can be downloaded from the course website.

```
.MODEL CMOSN NMOS (
+ TOX    = 5.75E-9      NSUB    = 1E17      LEVEL   = 3
+ PHI    = 0.7          VTO     = 0.4238252  GAMMA    = 0.4317311
+ UO     = 425.6466519  ETA     = 0          DELTA    = 0
+ KP     = 2.501048E-4  VMAX   = 8.287851E4    THETA    = 0.1754054
+ RSH    = 4.062439E-3  NFS     = 1E12        KAPPA    = 0.1686779
+ XJ     = 3E-7         LD      = 3.162278E-11  TPG      = 1
+ CGDO   = 3.1E-10      CGSO    = 3.1E-10      WD       = 1.23288E-8
+ CJ     = 2.0E-3       PB      = 0.9         CGBO    = 0
+ CJSW   = 2.8E-10      MJSW    = 0.44        MJ       = 0.5
                                PBSW    = 0.9)
```


```

.MODEL CMOSF PMOS (
+ TOX    = 5.75E-9      NSUB    = 1E17      LEVEL   = 3
+ PHI    = 0.7          VTO     = -0.5536085  GAMMA   = 0.6348369
+ UO     = 250          ETA     = 0          DELTA   = 0
+ KP     = 5.194153E-5  VMAX   = 2.295325E5  THETA   = 0.1573195
+ RSH    = 30.0776952   NFS     = 1E12      KAPPA   = 0.7448494
+ XJ     = 2E-7         LD      = 9.968346E-13 TPG     = -1
+ CGDO   = 2.70E-10     CGSO    = 2.7E-10      WD      = 5.47511E-9
+ CJ     = 1.9E-3       PB      = 0.9        CGBO    = 0
+ CJSW   = 2.2E-10     MJSW    = 0.32      MJ      = 0.48
                                   PBSW    = 0.9)

```

Table 2.1 Required Capacitances		
	NMOS	PMOS
$C_{db}$ high-to-low		
$C_{db}$ low-to-high		
$C_{gc}$		
$C_{gd}$		


b) Figure 2.2 displays an alternative layout design of a transistor, often referred to as a “folded” layout. It is similar to a pair of transistors connected in parallel to a common drain node. Using the  $K_{eq}$ ,  $C_j$ , and  $C_{jsw}$  calculated in part A, compare the capacitances  $C_{db}$ ,  $C_{gc}$ , and  $C_{gd}$  with the conventional layout. Do this for the high-to-low transition of an NMOS device only. You may assume that  $L_s$  for the folded layout is equal to  $2.5 \cdot L_{drawn}$ . What is a possible advantage of this structure, given that it will provide an equal amount of drain current to the conventional design?

 

**Figure 2.1** Conventional Layout

**Figure 2.2** Folded Layout

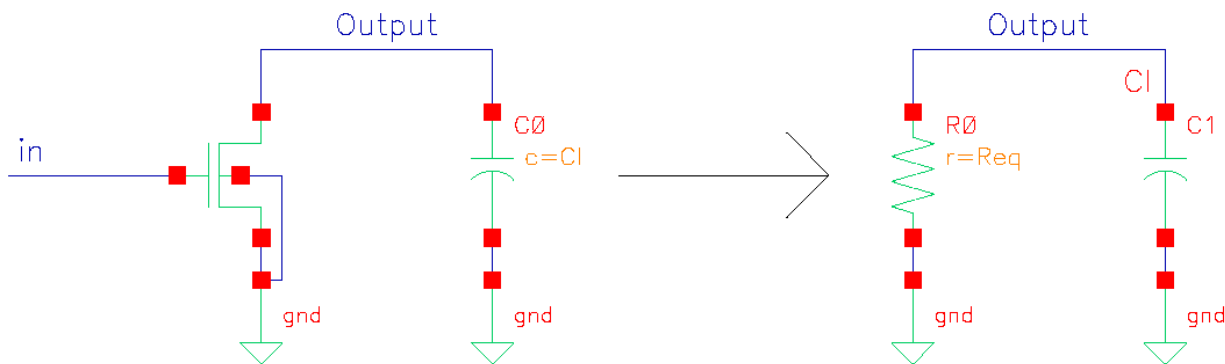3. a) As a circuit designer, you control a block of a large scale design in a product that is nearing a time-to-market deadline. The design is targeted to reach 1.2 GHz, optimistically, and the circuit must reach 95% of its final voltage on a falling transition within the clock cycle. The circuit in question is modeled by a simple first-order RC network with a fanout of 3 identical gates with each having 24.4 fF of input capacitance. Find the maximum acceptable value for  $R_{eq}$  in the circuit below.
- b) Three days later, a fellow engineer mentions that the fanout of your circuit has increased to 3 identical gates with each having 28.3 fF of input capacitance. The minimum acceptable frequency for market profitability is 1GHz. Will the product be able to meet the minimum performance goal with the increased fanout while using the previously calculated  $R_{eq}$ ? Show all calculations used to make this judgment.



This simple circuit can be modeled by a first-order RC network for the purposes of this problem.

4. Given Table 4.1, the goal of this problem is to derive important device parameters from these data points. As the measured transistor is processed in a deep-submicron technology, the '**unified model**' holds. From the material constants, we also could determine that the saturation voltage  $V_{DSAT}$  is equal to -1 V. You may also assume that  $-2\Phi_F = -0.6V$ . **NOTE: The parameter values on Table 3.3 do NOT hold for this problem.** (Hint: You will be working with the 'unified model' in many situations this semester, it may be worth your time to setup a file in Matlab or Excel to assist with these calculations.)
- Is the measured transistor a PMOS or an NMOS device? Explain your answer.
  - Determine the value of  $V_{T0}$ .
  - Determine  $\gamma$ .
  - Determine  $\lambda$ .
  - Given the obtained answers, determine for each of the measurements the operation region of the transistor (choose from *cutoff*, *linear*, and *saturation*). Annotate your finding in the right-most column of table 4.1.

**Table 4.1:** Measurements taken from MOS devices at various terminal voltages.

Measurement number	VGS (V)	VDS (V)	VSB (V)	ID ( $\mu$ A)	Operation Region?
1	-2.5	-2.5	0	-84.375	
2	1	1	0	0.0	
3	-0.7	-0.8	0	-1.04	
4	-2.0	-2.5	0	-56.25	
5	-2.5	-2.5	-1	-72.0	
6	-2.5	-1.5	0	-80.625	
7	-2.5	-0.8	0	-66.56	