

Graph

Description

This example uses a potentiometer as an input device and the serial monitor to display the value of the potentiometer. We will be using the code provided under the examples on the Arduino* IDE 1.5.3.

Hardware

- Intel® Galileo
- Breadboard
- Potentiometer
- Wires

Instructions

1. Place the potentiometer on the breadboard. *(see circuit below)*
2. Connect pin 1 on the potentiometer to GND on the Galileo board. *(see circuit below)*
3. Connect pin 2 on the potentiometer to A0 on the Galileo board. *(see circuit below)*
4. Connect pin 3 on the potentiometer to 5V on the Galileo board. *(see circuit below)*
5. Connect power supply to the Galileo and USB to USB Client Port on the Galileo.
6. Open Arduino IDE under Tools → Board select Intel® Galileo
7. Under Tools → Serial Port select the Com # where the Galileo is connected to.
8. Under File → Examples → 04.Communication and select the “Graph” example.
9. Upload to the Galileo by clicking the upload button. 
10. Monitor the value of the potentiometer in the Serial Monitor. 

Circuit

